

Project Update

Team #302: Asynchronous Ballistic Reversible Superconducting (ABRS) Computing
Frank Allen, Oscar Lopez, James Hardy, and Fadi Matloob

Agenda



- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress

Outline

- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress

Project Scope

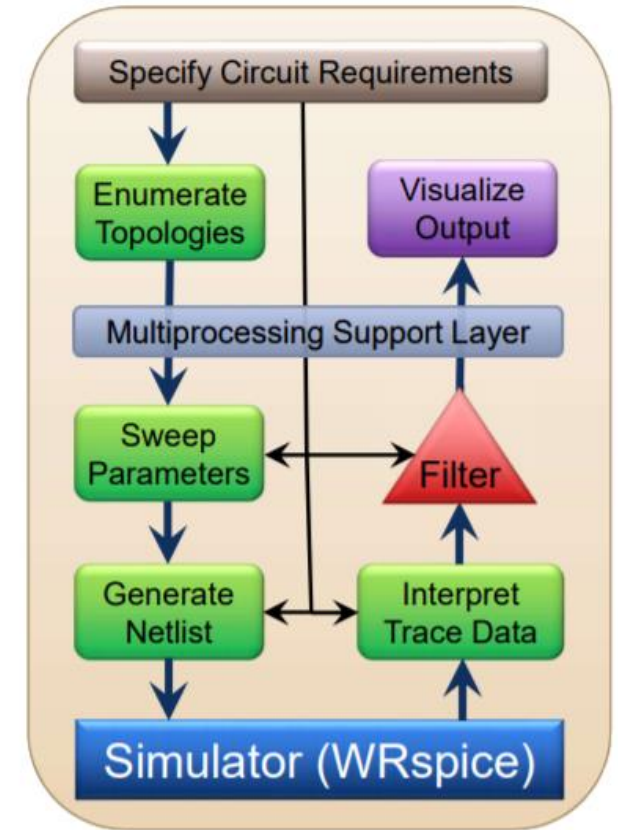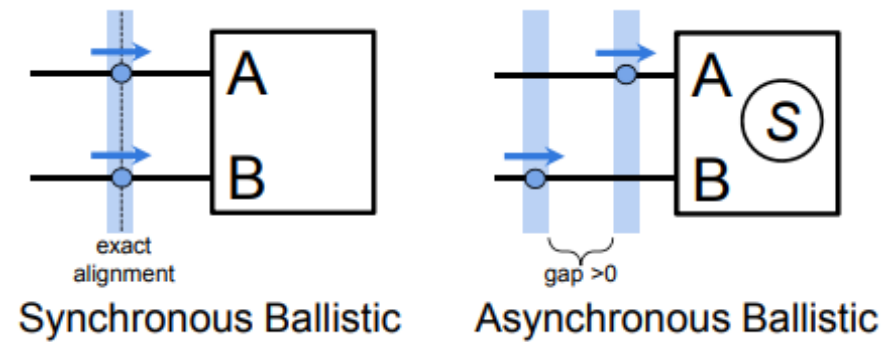- Project Goal:
 - Create a software tool to find functioning asynchronous reversible superconducting circuits
- Key Requirements:
 - Generate Circuit Topologies
 - Sweep Possible Device Values
 - Interpret and Filter the Results
 - Visualize Functional Circuits




Fadi Matloob

Outline

- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress

Functional Decomposition Cont.

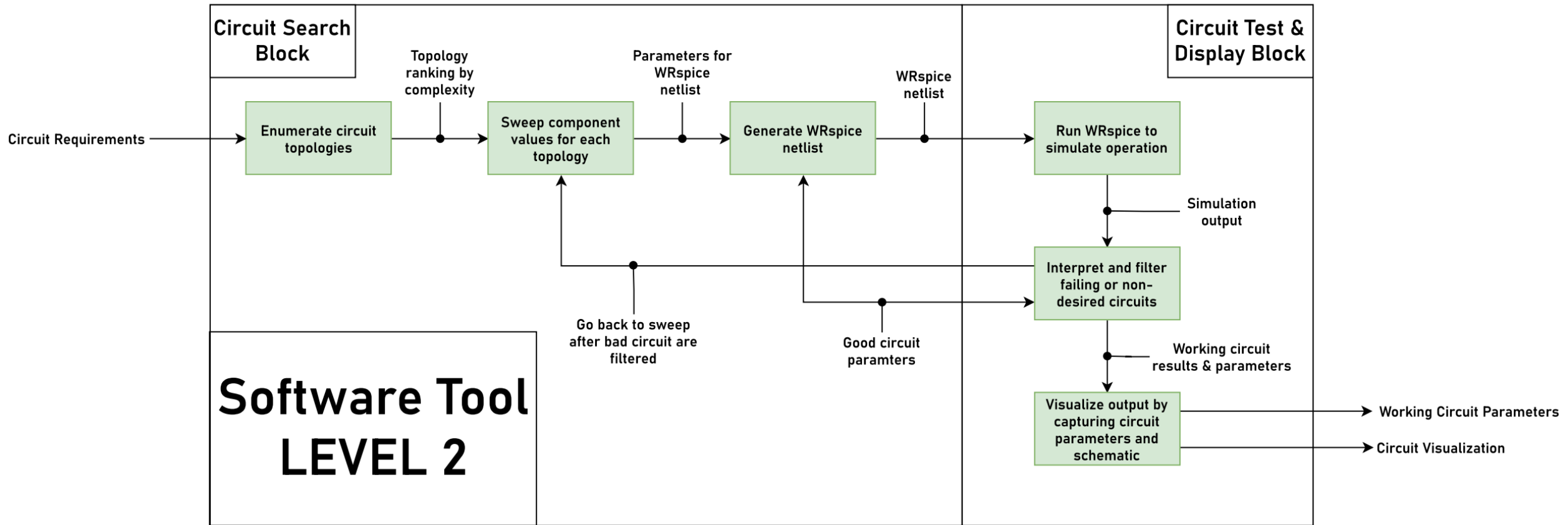

Fadi Matloob


Outline

- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress

James Hardy




Walking Through Components – Clickable

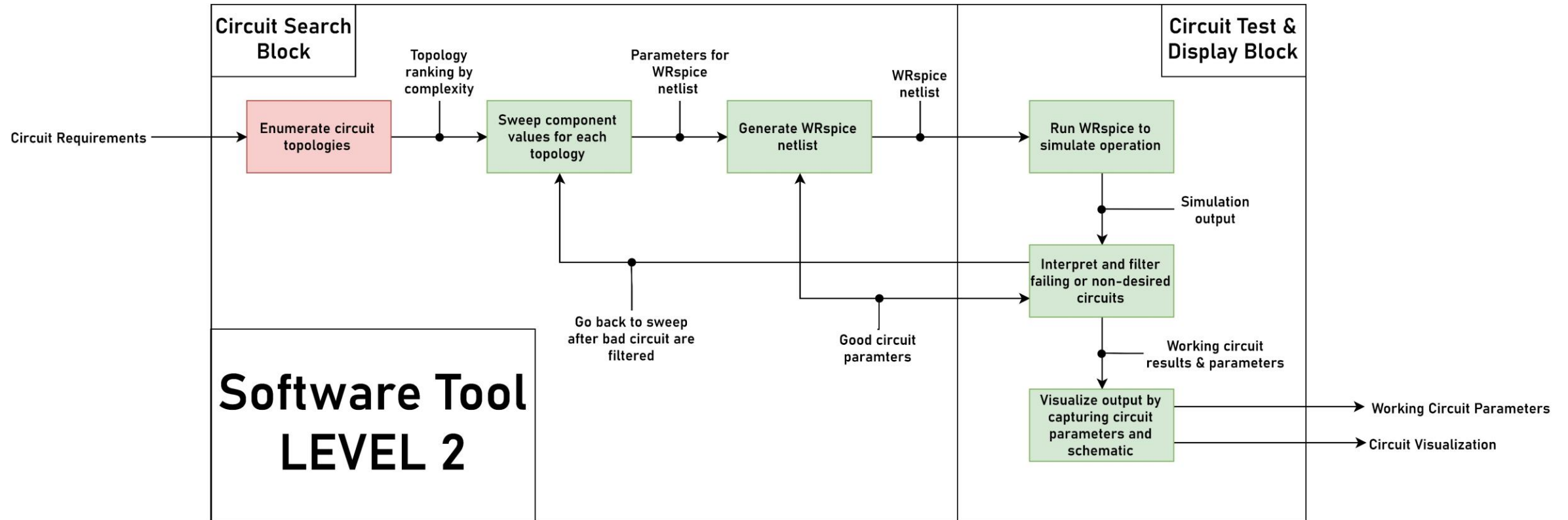


James Hardy

Walking Through Components Cont.

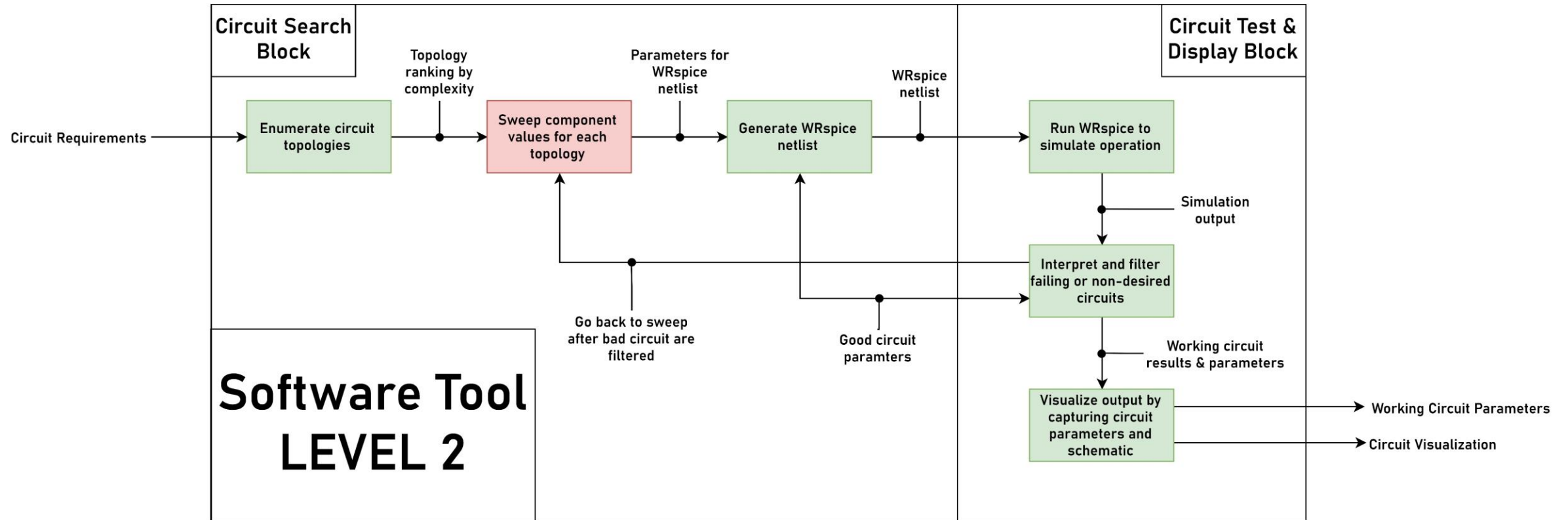


James Hardy

Walking Through Components Cont.

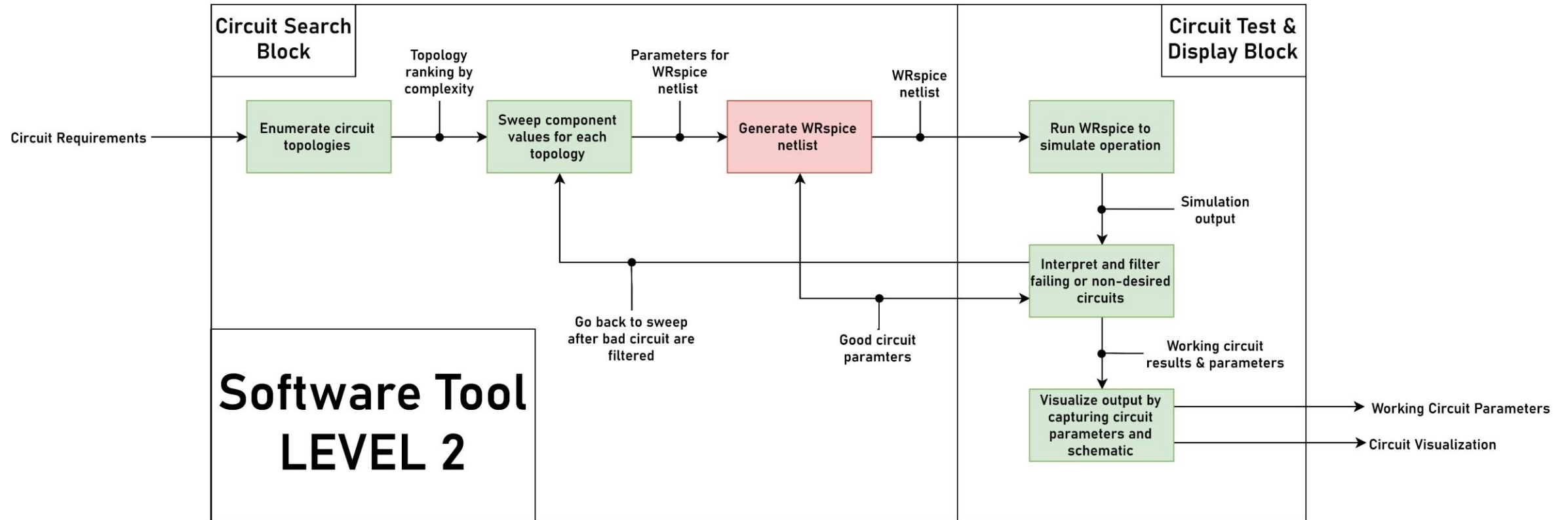


Frank Allen

Walking Through Components Cont.

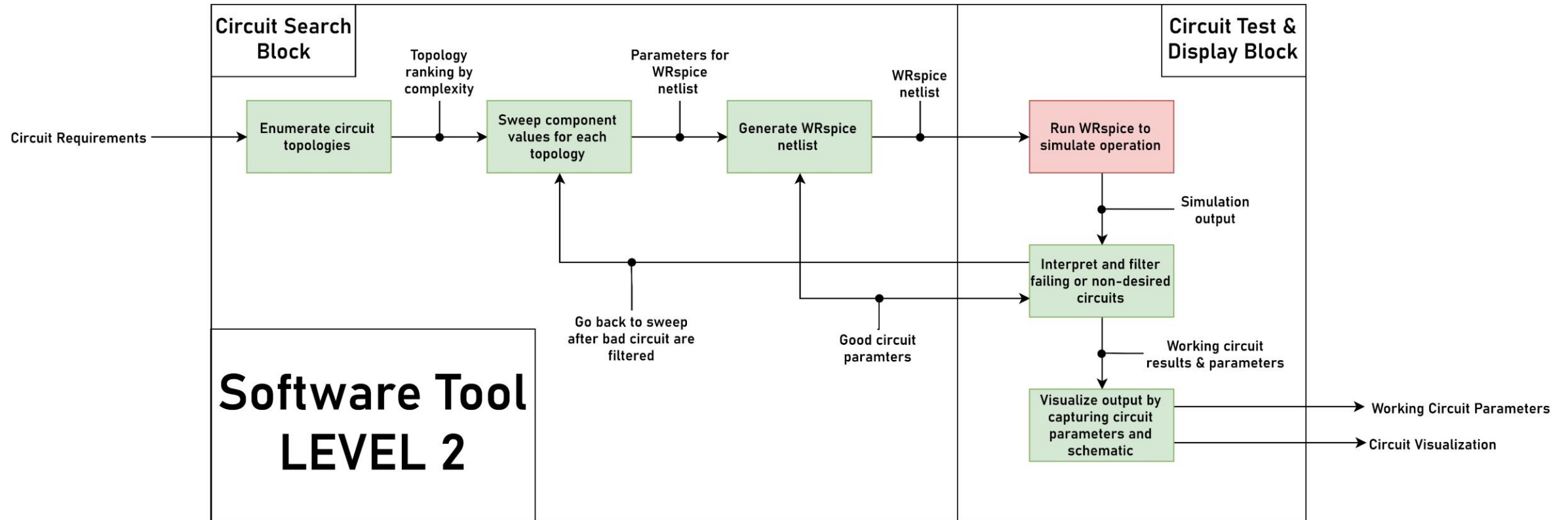


Frank Allen

Walking Through Components Cont.

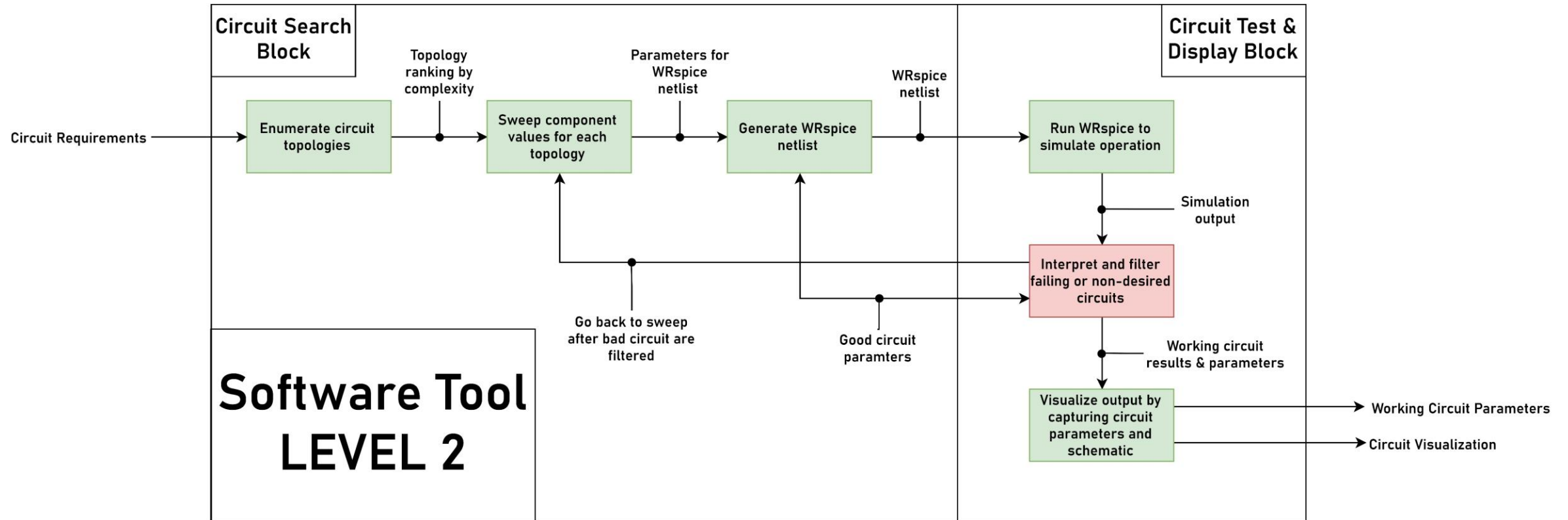

Oscar Lopez

Walking Through Components Cont.

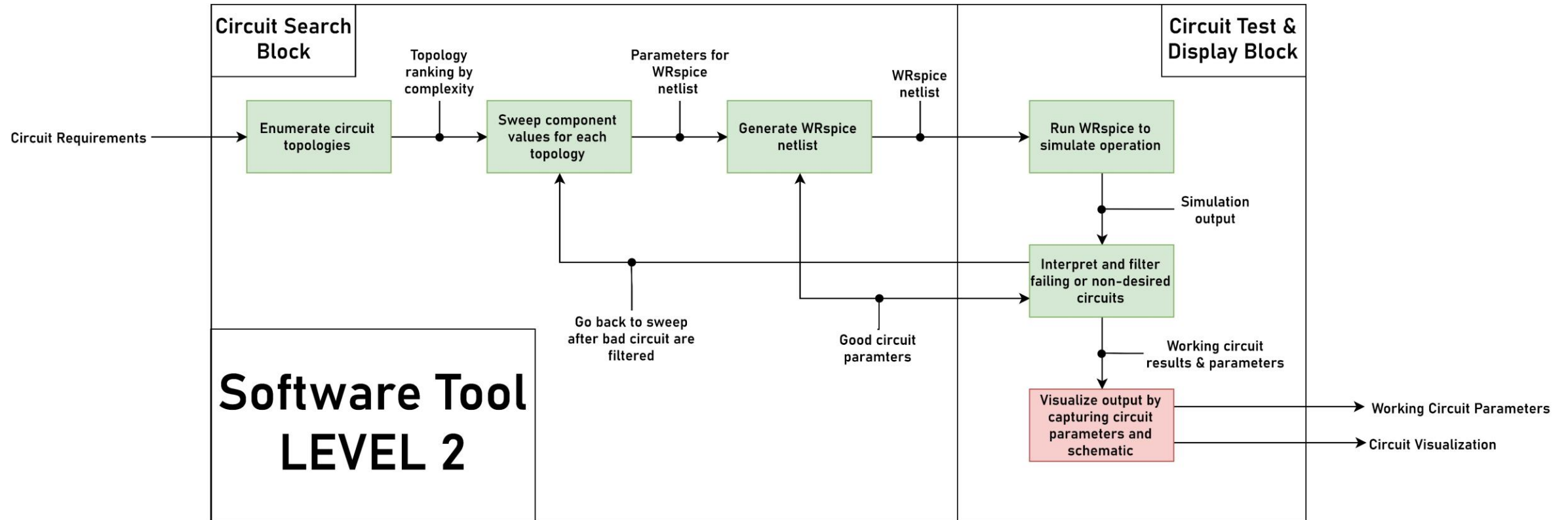

Oscar Lopez

Outline


- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress

Frank Allen




Bugs & Difficulties

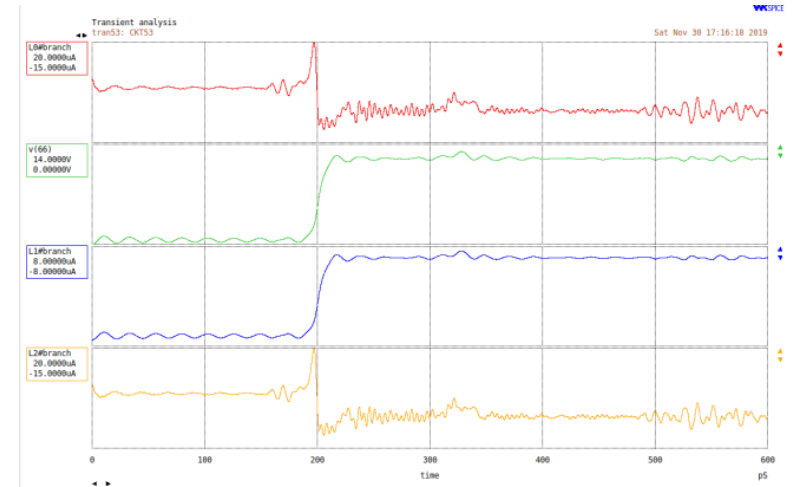- Combinational circuits
 - Series & Parallel
- Sweeping values
 - Algorithm
- Simulation
 - Matching output
 - Testing automation
- Filtering results
 - Fluxon existence only



Generated Circuit

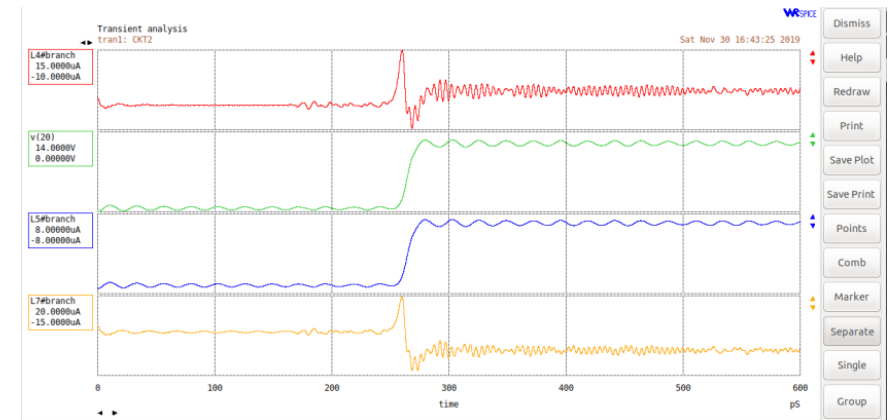

Existing Circuit

Frank Allen

Outline

- Summary
 - Project Scope
 - Function Decomposition
- Progress Breakdown
 - Walking Through Components
- Challenges
 - Bugs & Difficulties
- Next Steps
 - Plan For Progress


Plan For Progress

- Discussion with Michael Frank
 - Matching output
- Testing and validation
 - Parallel processing
- Visual output

Fadi Matloob



Code

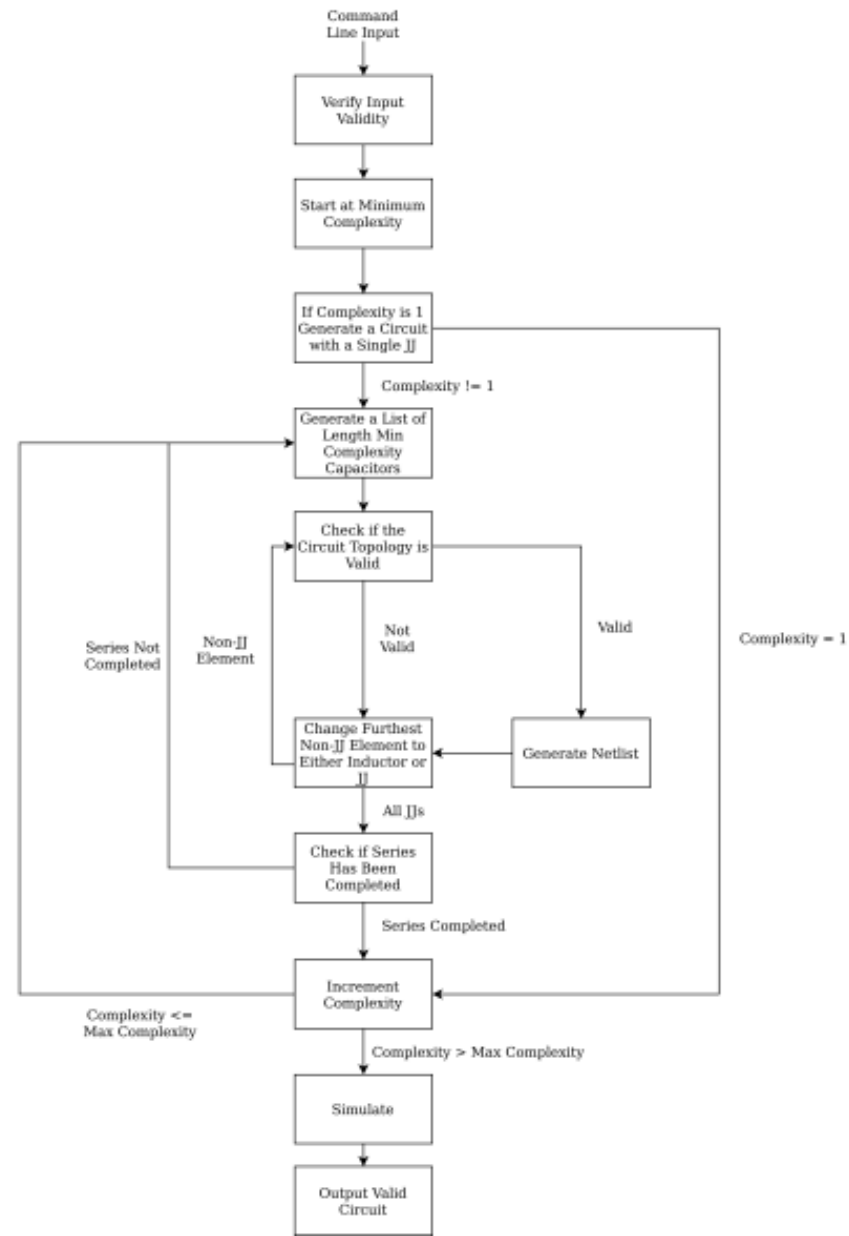



Frank Allen

Netlist Example - Clickable

```
.lib C:\Users\FaDiMaT\Downloads\XIC\main.lib master
.model jjk2 jj(rtype=0, cct=1, vg=2.8m, icrit=1.5u, cap=60f)
```

```
.tran 0.02ps 0.6ns uic
```

```
x0 aa zz master
```

```
L0 aa a 0H
L1 aa zz 300pH ic=-7uA
L2 b zz 0H ic=-7uA
B0 a b 66 jjk2 ics=7.5uA
```

```
.save tran L0#branch v(66) L1#branch L2#branch
```

```
.control
run
plot L0#branch v(66) L1#branch L2#branch
write outtest2 L0#branch v(66) L1#branch L2#branch
.endc
```

```
*****
* TEAM 302
* Lib file
* Contents:
*   - DCSFQ
*     - Purpose:
*       - Convert DC current to Single Fluxon Quantum
*       - Pluse
*     - Schematic provided by SUNY
*       - physics.sunysb.edu/Physics/RSFQ/Lib/AR/dcsfq.html
*   - LJJ
*     - Purpose:
*       - Transmission line, forces delay
*     - Schematic provided by Sandia Labs
*   - 20LJJ
*     - Purpose:
*       - 20 LJJ's
*       - spaced so proding can be done
*       - makes it easier to do a complete 100
*     - Piecewise Current source
*       - Needed for the DCSFQ input
*****
```

```
.lib master
.subckt master top_out bottom_out



.model jjk jj(rtype=0, cct=1, vg=2.8m, icrit=1.5u, cap=60f)
I0 0 top1 pwl(0 0 25p -0.87n 75p 0.35n 900p 0 r)
X0 top1 top2 20uAdcsfq
L0 top2 top3 150pH ic=13.7855589uA
X1 top3 0 top4 bottom1 dljj20
X2 top4 bottom1 top5 bottom2 dljj20
X3 top5 bottom2 top6 bottom3 dljj20
X4 top6 bottom3 top7 bottom4 dljj20
X5 top7 bottom4 top_out bottom_out dljj20

.subckt dljj-seg LT LB RT RB
.model jjk jj(rtype=0, cct=1, vg=2.8m, icrit=1.5u, cap=60f)
B0 5 6 7 jjk ics=1.5uA
L0 LT 5 7.845pH
L1 5 RT 7.845pH
L2 LB 6 7.845pH
L3 6 RB 7.845pH
.ends dljj-seg

.subckt dljj20 LT LB RT RB
X0 LT LB 5 25 dljj-seg
X1 5 25 6 26 dljj-seg
X2 6 26 7 27 dljj-seg
X3 7 27 8 28 dljj-seg
X4 8 28 9 29 dljj-seg
X5 9 29 10 30 dljj-seg
X6 10 30 11 31 dljj-seg
X7 11 31 12 32 dljj-seg
X8 12 32 13 33 dljj-seg
X9 13 33 14 34 dljj-seg
X10 14 34 15 35 dljj-seg
X11 15 35 16 36 dljj-seg
X12 16 36 17 37 dljj-seg
X13 17 37 18 38 dljj-seg
X14 18 38 19 39 dljj-seg
X15 19 39 20 40 dljj-seg
X16 20 40 21 41 dljj-seg
X17 21 41 22 42 dljj-seg
X18 22 42 23 43 dljj-seg
X19 23 43 RT RB dljj-seg

```

WRspice Example

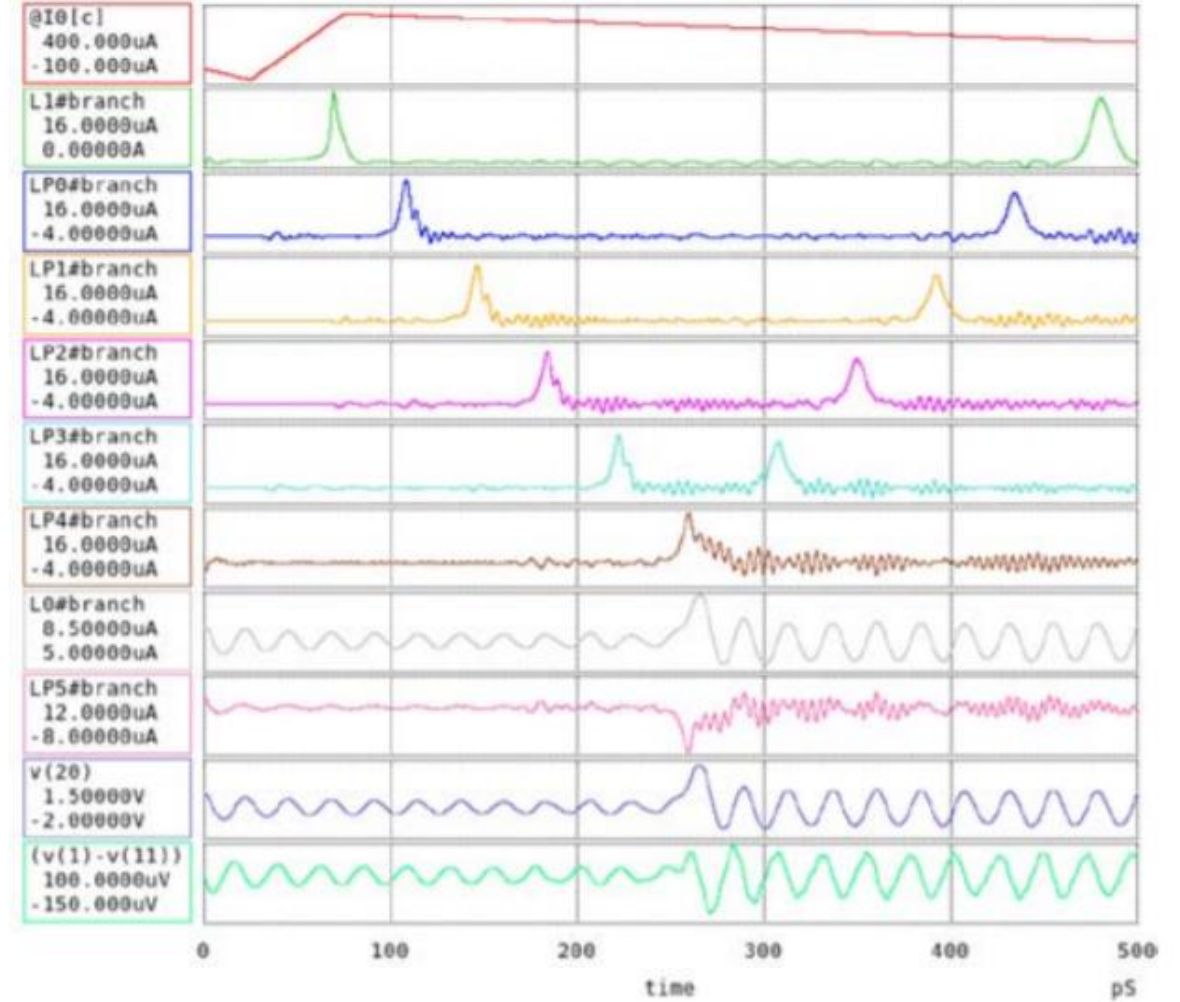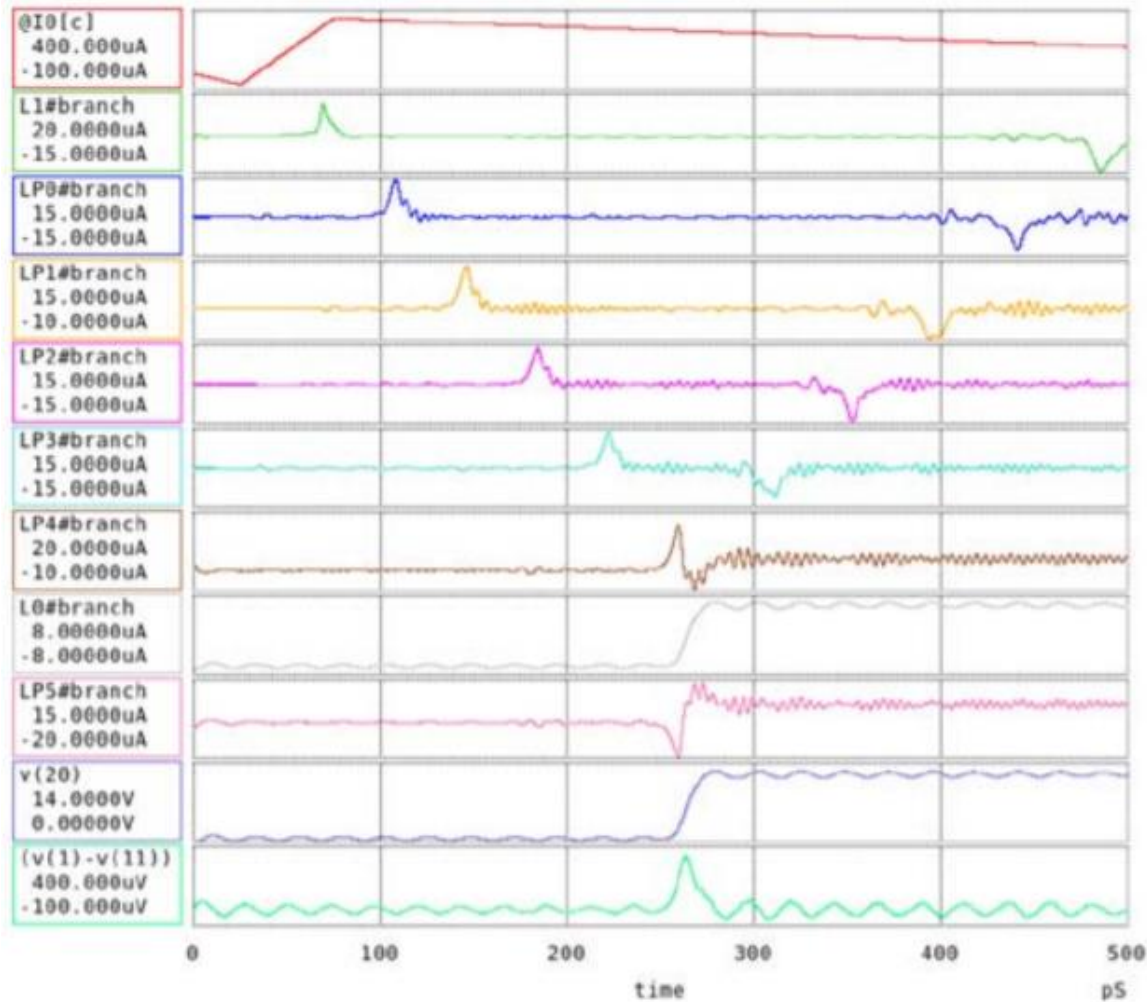

Visual Example

