




FAMU-FSU
College of Engineering



Lecture #2: Circuit Fundamentals

EEL 3003
Introduction to Electrical Engineering
Summer Semester, 2013
Instructor: Dr. Michael Frank

5/18/2013 (v1.1) M. Frank, EEL 3003 - Intro. EE, Summer 2013 1




FAMU-FSU College of Engineering

Administrative Announcements

- Today's Handouts:
 - Attendance sheet – please sign, & correct your data.
 - Finalize your registration status by tomorrow!
- Outline of Today's Lecture:
 1. Review practice problems I posted yesterday.
 2. Overview of Chapter 2 –
 - Fundamentals of Electric Circuits
 3. Begin in-depth coverage of chapter 2.
- Today's Homework Assignment:
 - Read Ch. 2 of Textbook (Rizzoni 5th ed.)
 - Practice exercises:
 - Attempt the following homework problems (randomly selected):
 - 2.8, 2.19, 2.26*, 2.36, 2.37, 2.51*, 2.57, 2.64*, 2.73, 2.77
 - Starred problems have solutions in the back of the book.
 - You may also want to attempt additional problems that have solutions printed in the back of the book.
 - The related quiz will be next Thursday (May 23rd).

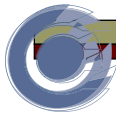5/18/2013 (v1.1) M. Frank, EEL 3003 - Intro. EE, Summer 2013 2



Overview of Chapter 2 (Fundamentals of Electric Circuits)

- | | |
|---|---|
| §2.1 – Definitions | §2.5 – Circuit Elements
and their i - v
Characteristics |
| §2.2 – Charge, current, &
Kirchhoff's Current
Law | §2.6 – Resistance and
Ohm's Law |
| §2.3 – Voltage &
Kirchhoff's Voltage
Law | §2.7 – Practical Voltage &
Current Sources |
| §2.4 – Electric Power and
Sign Convention | §2.8 – Measuring Devices |



Section §2.1 – Definitions


- | | | |
|--|--|---|
| <ul style="list-style-type: none"> □ Circuit topology terms: <ul style="list-style-type: none"> ■ Wire ■ Terminal ■ Port ■ Source ■ Load ■ Branch ■ Junction ■ Node <ul style="list-style-type: none"> □ Supernode ■ Loop <ul style="list-style-type: none"> □ Simple loops, figure-8's ■ Mesh | | <ul style="list-style-type: none"> □ Ideal Sources: <ul style="list-style-type: none"> ■ Ideal Voltage Sources ■ Ideal Current Sources □ Dependent (Controlled) Sources: <ul style="list-style-type: none"> ■ VCVS, CCVS, VCCS, CCCS |
|--|--|---|




Terminals and Ports

- Interconnections between electrical subcircuits can be described in terms of *wires*, *terminals* and *ports*.

(click slide to animate)

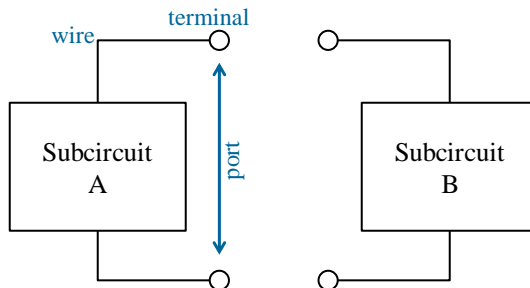

5/18/2013 (v1.1)

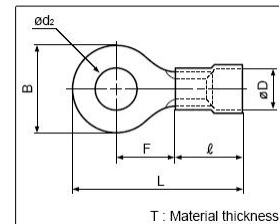


Ring tongue terminal products




M. Frank, EEL 3003 - Intro. EE, Summer 2013

5

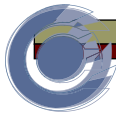

Sources vs. Loads

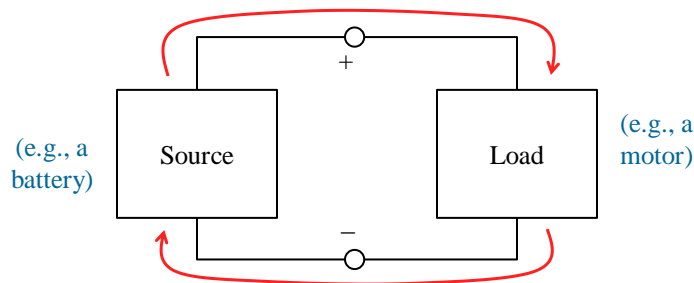
- A given subcircuit could be acting as either a *source* or a *load* depending on whether it is supplying (positive) power to other components, or consuming power delivered to it by other components.
 - Source: Positive current flows *out* of its high-voltage terminal
 - Load: Positive current flows *into* its high-voltage terminal



5/18/2013 (v1.1)


M. Frank, EEL 3003 - Intro. EE, Summer 2013

6

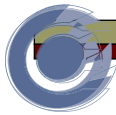


Ideal Voltage Sources


- Some variants:

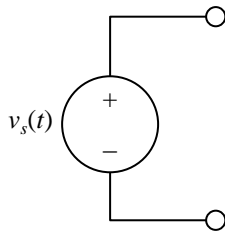

General time-dependent
voltage source

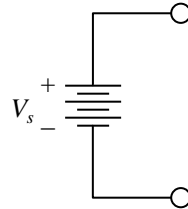

DC voltage source
(an ideal battery)

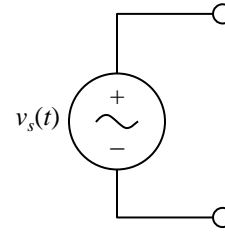


Sinusoidal AC
voltage source

5/18/2013

(v1.1)


M. Frank, EEL 3003 - Intro. EE, Summer 2013

7

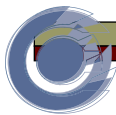


Ideal Current Sources

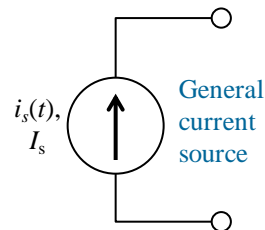- Generally more difficult to approximate in practice than ideal voltage sources.
 - However, many different methods for constructing approximate current sources are known.



General
current
source

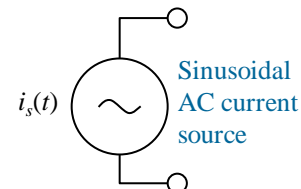


Sinusoidal
AC current
source

5/18/2013 (v1.1)



M. Frank, EEL 3003 - Intro. EE, Summer 2013

8

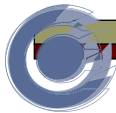

Dependent (Controlled) Sources

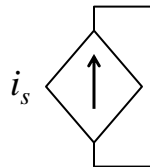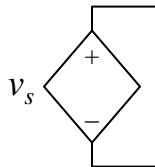
- Four basic types:
 - VCVS – Voltage Controlled Voltage Source
 - CCVS - Current Controlled Voltage Source
 - VCCS – Voltage Controlled Current Source
 - CCCS – Current Controlled Current Source



5/18/2013 (v1.1)

M. Frank, EEL 3003 - Intro. EE, Summer 2013

9

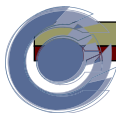


Some More Network Terminology

- | | |
|--|---|
| <ul style="list-style-type: none"> □ Component (a.k.a. device) <ul style="list-style-type: none"> ■ A minimal element of a circuit diagram, other than an ideal wire ■ Needs 2 or more terminals to be useful in a circuit □ Wire <ul style="list-style-type: none"> ■ a direct connection between two points (device terminals or junctions) ■ Treated as an ideal conductor □ Junction (a.k.a. join, solder dot) <ul style="list-style-type: none"> ■ A point of connection between 2 or more wires ■ Treated as an ideal conductor ■ A junction and all wires incident <u>on it</u> are part of the <u>same</u> node | <ul style="list-style-type: none"> □ Node <ul style="list-style-type: none"> ■ A <u>maximal</u> connected set of wires and junctions. ■ A maximal ideally-conductive region, which may have any number of circuit branches incident on it. □ Circuit <ul style="list-style-type: none"> ■ A maximal connected set of wires, devices & joins □ Subcircuit <ul style="list-style-type: none"> ■ A connected subset of a circuit. □ Terminal <ul style="list-style-type: none"> ■ A designated entry/exit point of a device or subcircuit, on a wire crossing its boundary ■ May be considered a type of junction (when connected) |
|--|---|

5/18/2013 (v1.1)


M. Frank, EEL 3003 - Intro. EE, Summer 2013

10

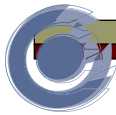


Even more terminology...

- Supernode
 - Any subcircuit with two or more terminals
- Branch
 - Most generally: Any supernode with exactly 2 terminals
 - Often comprises a maximal linear chain of devices
 - Branches may, however, contain loops inside them
- Minimal branch
 - A single 2-terminal device
- Loop
 - A cycle (cyclical sequence) of connected branches & nodes
- Simple Loop
 - Includes no node more than once.
- “Figure Eight”
 - A (non-simple) loop that includes 1 node exactly twice.
- Mesh
 - A loop that has no smaller loops inside it.
 - No “short cut” across the loop.

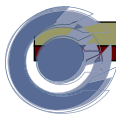

Terminology Example

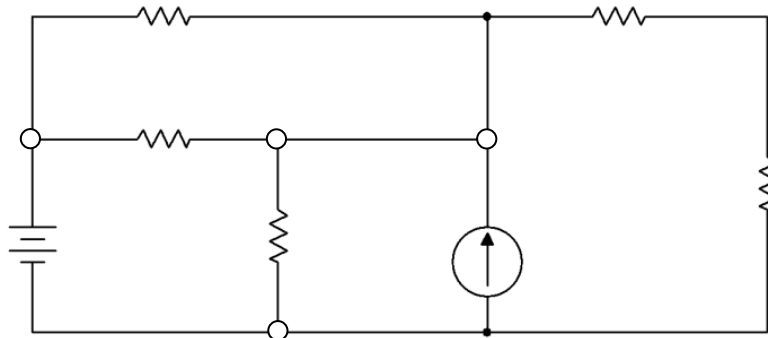- Exercise (in-class or at-home):
 - Identify & count all of the following items in this circuit:
 - Components, wires, indicated terminals, junctions, subcircuits, nodes, supernodes, branches, meshes, simple loops, figure-8's





Counting the Loops

- The caption on figure 2.8 says that this circuit has 15 loops, but really, to be more precise:
 - It has only 10 simple loops.
 - It also has 5 figure eights.
 - Highlighted in yellow on next slide
 - It also includes several additional loops (not shown on next slide) in which more than one node is included more than once
 - If you're bored, see if you can count all of those...

5/18/2013 (v1.1)

M. Frank, EEL 3003 - Intro. EE, Summer 2013

13

