



FAMU-FSU
College of Engineering




Lecture #6:
Resistive Network Analysis
(Part III)

EEL 3003
Introduction to Electrical Engineering
Summer Semester, 2013
Instructor: Dr. Michael Frank

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 1




FAMU-FSU College of Engineering



Administrative Announcements

- Outline of Today's Lecture:
 1. Continue Chapter 3, Resistive Network Analysis
 - §3.4 – Node & mesh analysis w. Controlled sources
 - §3.5 – Principle of Superposition
 - §3.6 – Norton/Thevenin Equivalent Circuits
 - §3.7 – Maximum Power Transfer Theorem
 - §3.8 – Nonlinear Circuit Elements ← light coverage
- Reminder: Current Homework Assignment:
 - Read Ch. 3 of Textbook (Rizzoni 5th ed.)
 - Practice exercises:
 - 3.6, 3.10, 3.17, 3.43, 3.60, 3.72, 3.74*, 3.75, ~~3.76, 3.81~~ ← last 2 optional
 - Quiz Tuesday (June 4th).

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 2




FAMU-FSU College of Engineering

Continue Chapter 3, Resistive Network Analysis

- ☐ §3.1 Network Analysis
- ☐ §3.2 The Node Voltage Method
- ☐ §3.3 – The Mesh Current Method
 - See supplemental notes I posted after last lecture
- ☐ §3.4 – Node & mesh analysis w. Controlled sources
- ☐ §3.5 – Principle of Superposition
- ☐ §3.6 – Norton/Thévenin Equivalent Circuits
- ☐ §3.7 – Maximum Power Transfer Theorem
- ☐ §3.8 – Nonlinear Circuit Elements – covering lightly

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 3



FAMU-FSU College of Engineering

§3.4 – Node & Mesh Analysis with Controlled Sources

- ☐ Each controlled source gives us a *constraint equation* which we plug into the analysis.
 - Gives controlled value of voltage or current in terms of controlling voltage or current.
 - ☐ Does not increase number of unknowns, since controlled value is completely determined by controlling value.
- ☐ Let's quickly go through the example in the textbook...

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 4

FAMU-FSU College of Engineering

Example of Node/Mesh Analysis with Controlled Sources

□ Consider this circuit (from fig. 3.24, p. 101):

What type of source do we have here?

What's easier in this circuit, node or mesh analysis? Why?

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 5

FAMU-FSU College of Engineering

Fig. 3.24 Example, continued


□ KCL equation for Node 1:

$$i_s = v_1 \left(\frac{1}{R_s} + \frac{1}{R_b} \right) \quad (\text{eq. 1})$$

□ KCL equation for Node 2:

$$\beta i_b + \frac{v_2}{R_c} = 0 \quad (\text{eq. 2})$$

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 6



FAMU-FSU College of Engineering




Fig. 3.24 Example, continued

- Next, use current-divider rule to express the controlling current i_b in terms of i_s :

$$i_b = i_s \frac{1/R_b}{1/R_b + 1/R_s} = i_s \frac{R_s}{R_b + R_s} \quad (\text{eq. 3})$$


- So, the controlled current is:

$$\beta i_b = \beta i_s \frac{R_s}{R_b + R_s} \quad \left. \vphantom{\beta i_b} \right\} \begin{array}{l} \text{Constraint} \\ \text{equation} \end{array} \quad (\text{eq. 4})$$

5/30/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

7



FAMU-FSU College of Engineering




Fig. 3.24 example, cont.

- Plug constraint equation back into the KCL equation that involved the controlled current source (eq. 2):

$$\beta i_s \frac{R_s}{R_b + R_s} + \frac{v_2}{R_C} = 0 \quad (\text{eq. 5})$$


- Thus, v_2 can be solved in terms of i_s :

$$v_2 = -\beta i_s \frac{R_s R_C}{R_b + R_s} \quad (\text{eq. 6})$$

5/30/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

8



FAMU-FSU College of Engineering





Fig. 3.24 example, cont.

- Here both v_1 & v_2 are solved in terms of i_s :


$$v_1 = \frac{i_s}{1/R_s + 1/R_b} \quad (\text{eq. 7})$$

$$v_2 = -\beta i_s \frac{R_s R_C}{R_b + R_s} \quad (\text{eq. 6 again})$$
- So, if the independent source current i_s , the coefficient β , & the R 's are given, we're done.

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
9




FAMU-FSU College of Engineering




§3.5 – The Principle of Superposition

- In a linear circuit,
 - which means, one containing only linear devices,
 - which are: resistors, capacitors, & inductors,
- the effects of multiple sources are additive,
 - which means, the solution with multiple sources is just the sum of solutions found with individual sources...
 - you just have to simplify the multi-source circuits to single-source circuits in the right way.

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
10



FAMU-FSU College of Engineering




Rules for “Zeroing Out” Sources

- When simplifying a multiple-source circuit to a single-source circuit,
 - for purposes of later applying the Superposition Principle to combine your solutions,
- Set all of the *other* sources “equal to 0” in the following way:
 - Zero voltage source = closed (short) circuit.
 - Zero current source = open (disconnected) circuit.


5/30/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

11




FAMU-FSU College of Engineering



Simple Example of the Superposition Principle (from fig. 3.27, p. 106)

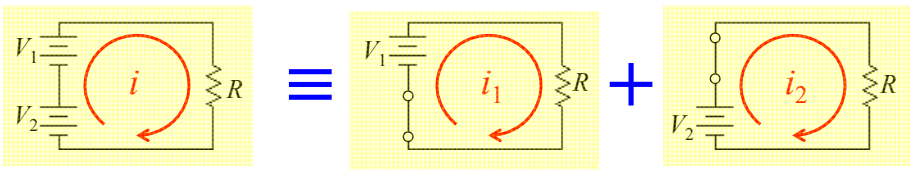- Voltage sources in series, with a single-resistor load.



$$i = \frac{V_1 + V_2}{R} = \frac{V_1}{R} + \frac{V_2}{R} = i_1 + i_2$$

5/30/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

12

FAMU-FSU College of Engineering

Slightly More Complicated Superposition Example (Fig. 3.28)

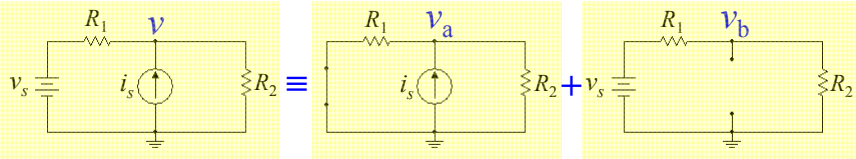□ Note current source gets replaced by an open circuit.



Currents on each branch of the circuit add (like in previous slide), therefore, because of Ohm's law, voltages on each node add as well, so:

$$v = v_a + v_b$$

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 13

FAMU-FSU College of Engineering

§3.6 – One-Port Networks & Equivalent Circuits

□ Recall that “one port” means “two terminals.”


- Thus, any subcircuit with exactly 2 terminals comprises a one-port network.

□ In a 1-port network w/o any reactance,

- which means, no capacitors or inductors,
 - only components like resistors/diodes,

□ the electrical properties of that network are completely described by its i/v characteristic,

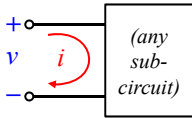- and the network can be described using a simplified *equivalent circuit* model.



5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 14

FAMU-FSU College of Engineering

Equivalent Circuits Example

- Gray box on left is a 2-terminal subcircuit (one-port network)
 - It is equivalent to the simplified circuit on the right.

The diagram shows two equivalent circuits. On the left, a voltage source v_S is connected to a gray box containing three parallel resistors R_1 , R_2 , and R_3 . The voltage across the box is v and the current entering is i . This is shown to be equivalent to a circuit with the same voltage source v_S connected to a gray box containing a single resistor R_{EQ} , with the same voltage v and current i .

$$R_{EQ} = 1/(1/R_1 + 1/R_2 + 1/R_3)$$

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 15

FAMU-FSU College of Engineering



Thévenin's Theorem

- Any 1-port network of ideal voltage & current sources & resistors is equivalent to a *single* ideal voltage source v_T in series with a *single* resistor R_T .
 - v_T is called the *Thévenin equivalent voltage* of the circuit.
 - Similarly, R_T is called the *Thévenin equivalent resistance*.

The diagram illustrates the theorem by showing a 'source network' connected to a 'load network'. The voltage across the load is v and the current is i . This is shown to be equivalent to a 'Thévenin equivalent circuit' consisting of a voltage source v_T in series with a resistor R_T , which is then connected to the same 'load network' with voltage v and current i .


Thévenin equivalent circuit

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 16


FAMU-FSU College of Engineering




Norton's Theorem

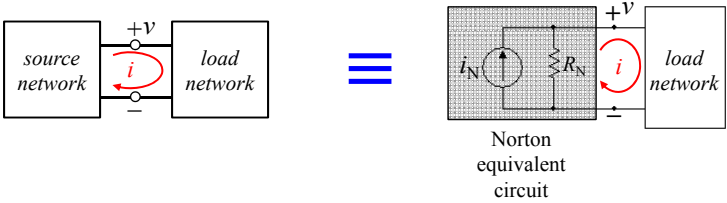- Any 1-port network of ideal voltage & current sources & resistors is equivalent to a single ideal *current* source i_N in *parallel* with a single resistor R_N .
 - i_N is called the *Norton equivalent current* of the circuit.
 - Similarly, R_N is called the *Norton equivalent resistance*.



Norton equivalent circuit

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
17


FAMU-FSU College of Engineering


Finding Thévenin/Norton Equivalent Circuits

This is rather easy!!!

- **Step 1:**
 - Set all sources equal to 0 and simplify to find the Thév./Norton equivalent resistance $R_T = R_N = R_{EQ}$.
- **Step 2:**
 - Thévenin voltage v_T = open-circuit voltage at output port (with load removed).
- **Step 3:**
 - Norton current i_N = short-circuit current at output port (shorting over the load)

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
18

FAMU-FSU College of Engineering

Equivalence of Thévenin & Norton Equivalent Circuits

- Since any one-port network has a Thévenin circuit & a Norton circuit that are both \equiv to the original network,
 - Obviously, therefore, the Thévenin circuit \equiv the Norton circuit.

- Thus, you can always transform a subcircuit that has only a voltage source & series resistor into one that has only a current source & parallel resistor, and vice-versa.

5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 19


FAMU-FSU College of Engineering

Response of a resistive load to a linear source

- When $R_L \gg R_{EQ}$, $v_L \rightarrow v_T$;
- When $R_L \ll R_{EQ}$, $i_L \rightarrow i_N$;
- When $R_L = R_{EQ}$, $v_L = v_T/2$ & $i_L = i_N/2$.
 - This is the maximum power point, $p = p_{max} = v_T i_N / 4$.
- See also supplemental note posted.


Load Voltage, Current, & Power for a Source with $R_{eq}=10\Omega$ and $V_T=10V$ or $I_N=1A$


5/30/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 20



FAMU-FSU College of Engineering

§3.7 – Maximum Power Transfer Theorem



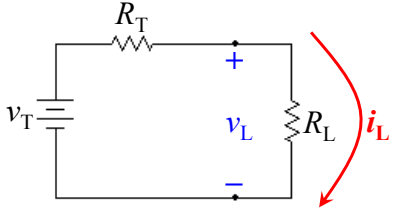


$$p_L = i_L^2 R_L \quad i_L = \frac{v_T}{R_T + R_L}$$

$$p_L = \frac{v_T^2 R_L}{(R_T + R_L)^2}$$


Let $\frac{dp_L}{dR_L} = 0$, (Steps on next slide) $\rightarrow R_L = R_T$.

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
21



FAMU-FSU College of Engineering

Full Derivation of MPTT Result




$$\frac{d}{dR_L} \frac{v_T^2 R_L}{(R_T + R_L)^2} = 0 \quad \frac{d}{dR_L} \frac{R_L}{(R_T + R_L)^2} = 0$$

$$\frac{d}{dR_L} R_L (R_T + R_L)^{-2} = R_L \frac{d}{dR_L} (R_T + R_L)^{-2} + (R_T + R_L)^{-2} \frac{d}{dR_L} R_L$$


$$= R_L (-2)(R_T + R_L)^{-3} + (R_T + R_L)^{-2} = \frac{1 - 2R_L / (R_T + R_L)}{(R_T + R_L)^2} = 0$$

$$1 - 2R_L / (R_T + R_L) = 0 \quad 2R_L = R_T + R_L \quad R_L = R_T$$

5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
22



FAMU-FSU College of Engineering




§3.8 – Nonlinear Circuit Elements

1. Description of Nonlinear Elements
 - Exponential i - v curve example (not yet covered)
2. Graphical (Load-Line) Analysis of Nonlinear Circuits
 - Discussed graphical method in class
 - (next slides)
 - Did not yet cover analytical solution examples
 - Homework problems optional
 - No quiz question on this topic this semester


5/30/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

23



FAMU-FSU College of Engineering



Equations to Calculate Source Loading

- Given any linear source (v_T, R_{EQ}) or (i_N, R_{EQ}),
 - To calculate the voltage v_L on the load given the current i_L through the load, or vice-versa:


$$v_L = v_T - i_L R_{EQ} = (i_N - i_L) R_{EQ}$$

$$i_L = i_N - v_L / R_{EQ} = (v_T - v_L) / R_{EQ}$$
 - This can be helpful for taking measurements of an unknown load using a known source.


5/30/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013


24



FAMU-FSU College of Engineering




Load-Line Equation

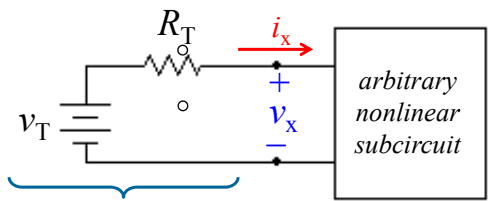

Thévinin equiv.
model of source

Useful to solve a circuit
with an arbitrary nonlinear
element (*e.g.*, diode) when
you only know its *i-v* curve.
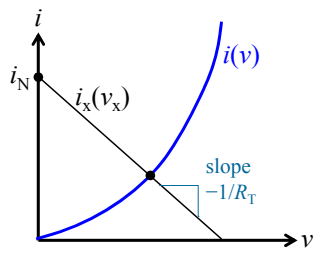
$$i_x = \frac{v_T - v_x}{R_T} = \left(\frac{v_T}{R_T} \right) - \left(\frac{1}{R_T} \right) v_x$$



5/30/2013
M. Frank, EEL 3003 - Intro. EE, Summer 2013
25