


FAMU-FSU
College of Engineering

Lecture #6:
AC Network Analysis

EEL 3003
Introduction to Electrical Engineering
Summer Semester, 2013

Instructor: Dr. Michael Frank

6/3/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 1




FAMU-FSU College of Engineering

Administrative Announcements

- Outline of Today's Class Session:
 1. Quiz #2 on Chapter 3, Resistive Network Analysis
 2. Start Chapter 4, AC Network Analysis
 - §4.1 – Energy Storage (Dynamic) Circuit Elements
 - §4.2 – Time-dependent Signal Sources
 - §4.3 – Solution of Circuits Containing Energy Storage Elements (Dynamic Circuits)
 - §4.4 – Phasor Solution of Circuits with Sinusoidal Excitation
 - §4.5 – AC Circuit Analysis Methods
- Announcing Homework Assignment #3:
 - Read Ch. 4 of Textbook (Rizzoni 5th ed.)
 - Practice by doing at least these 8 textbook exercises:
 - 4.1*, 4.12*, 4.31, 4.59*, 4.66, 4.68, 4.71, 4.77*
 - Quiz on this material next Tuesday (June 11th).

6/3/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 2



FAMU-FSU College of Engineering

Part I: Quiz #2 on Ch. 3
Resistive Network Analysis

- ½ hour for quiz
 - Please remain seated until time is up and I have collected all papers.
- Usual rules:
 - Calculator only

6/3/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 3

FAMU-FSU College of Engineering

Part II. Lecture: Start Ch. 4, AC Network Analysis

- §4.1 (pp. 150-167)
 - Energy Storage (Dynamic) Circuit Elements
- §4.2 (pp. 167-173)
 - Time-dependent Signal Sources
- §4.3 (pp. 173-175)
 - Solution of Circuits Containing Energy Storage Elements (Dynamic Circuits)
- §4.4 (pp. 175-191)
 - Phasor Solution of Circuits with Sinusoidal Excitation
- §4.5 (pp. 191-214)
 - AC Circuit Analysis Methods

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

4

FAMU-FSU College of Engineering

§4.1 - Energy Storage (Dynamic) Circuit Elements

- We'll study the following (ideal, linear, dynamic) elements:
 - Capacitors
 - Inductors

6/3/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

5

FAMU-FSU College of Engineering

Ideal Capacitors


- A capacitor stores charge,
 - and resists a *change in voltage*.
- For charge Q stored on a capacitor with capacitance C at voltage V : $Q = CV$.
 - Differential form: $C = dq/dv$.
- A capacitor is equivalent to an open circuit for a DC current.
 - Voltage can't build up indefinitely.
 - If I into a capacitor is *constant*, $I = 0$.
- Unit of capacitance: the *farad* (F)
 - $1 \text{ F} = 1 \text{ C/V}$

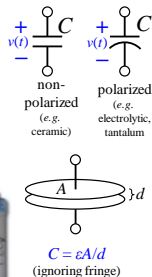1 Farad \rightarrow

6/3/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

6

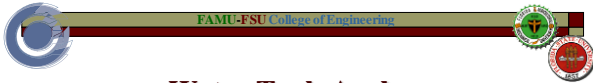

Water Tank Analogy

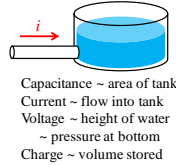- A rough analogue for a capacitor in a fluidic system is a storage tank for liquid
 - Fed by pipes at bottom of tank
 - Capacitance corresponds to area of tank
 - Constant capacitance = vertical tank walls
 - Gravity → height of water in tank is proportional to pressure at bottom of tank
 - Corresponds to voltage



6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

7



Relationship between current and voltage in a capacitor

- Starting from differential form of capacitor equation: $C = \frac{dq}{dv}$
- Derive:

$$C dv = dq$$

$$C \frac{dv}{dt} = \frac{dq}{dt}$$

$$i(t) = C \frac{dv}{dt} = C \dot{v}$$

Integral form:

$$v(t) = v(0) + \frac{1}{C} \int_{t'=0}^t i(t') dt'$$

6/3/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

8



Equivalent networks of capacitors

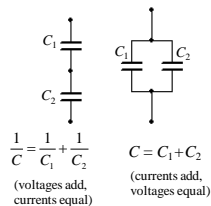- Series capacitors combine like parallel resistors,
 - And vice-versa.
- Because capacitance is current over (rate of change of) voltage
 - Whereas resistance is voltage over current
- The reciprocal of capacitance is called *elastance* (unit: “daraf”)



$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

(voltages add, currents equal)

$$C = C_1 + C_2$$

(currents add, voltages equal)

$$\frac{1}{C} = \frac{dv/dt}{i(t)} \quad C = \frac{i(t)}{dv/dt}$$

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

9



Energy Storage in Capacitors

- Energy stored when charging up a constant capacitor C from 0 V to voltage V :

$$\begin{aligned}
 E &= \int_{t=0}^T p(t) dt = \int_{t=0}^T i(t) \cdot v(t) dt \\
 &= \int_{t=0}^T C \frac{dv}{dt} \cdot v(t) dt = C \int_{v=0}^V v dv \\
 &= C \left(\frac{1}{2} v^2 \right) \bigg|_{v=0}^V = C \left(\frac{1}{2} V^2 \right) = \frac{1}{2} CV^2.
 \end{aligned}$$

Note:
Time is
irrelevant!

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

10



Capacitive Reactance

- This will be important later...
- Under an AC excitation with frequency f , a capacitor has a *reactance* of:

$$X_C = \frac{-1}{2\pi f C} \Omega$$

- The -1 in numerator \rightarrow a capacitor's voltage *lags* its current by a phase angle of $\pi/2$.
 - We'll discuss what this means later on...

6/3/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

11



Ideal Inductors

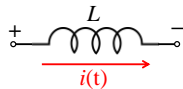- An inductor stores magnetic flux,
 - And resists a change in current
 - Equiv. to short-circuit for DC current
 - $v = \text{const.} \rightarrow v=0$.
- Unit: 1 Henry (H)
 - $1 \text{ H} = 1 \Omega \cdot \text{s}$




$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(0) + \frac{1}{L} \int_{t=0}^{t'} v(t') dt'$$

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

12

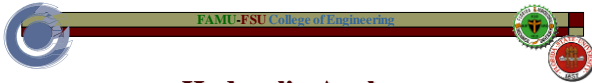

Hydraulic Analogy

- Inductance is analogous to *inertance* in fluidic systems
 - E.g. a low-viscosity liquid moving in a long coiled tube carries a lot of inertia (momentum)
 - Takes pressure applied over time to gradually accelerate the mass of liquid to higher flow rates
- Similarly, current moving in a coiled wire has an electrical analogue to momentum
 - Caused by the magnetic fields that form in the coil
 - It takes a voltage (electromotive force) applied over time to gradually “accelerate” the current to higher intensity

6/3/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

13




Equivalent networks of inductors

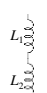- Series inductors combine like series resistors,
 - And parallel inductors like parallel resistors.
- Because inductance is voltage over (rate of change of) current
 - Resistance is voltage over current
- The reciprocal of inductance is called *reluctance* (unit: S/s)



$$L = L_1 + L_2$$

(voltages add,
currents equal)

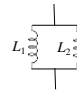

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$

(currents add,
voltages equal)

$$L = \frac{v(t)}{di/dt} \quad \frac{1}{L} = \frac{di/dt}{v(t)}$$

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

14



Energy Stored in an Inductor

- Energy stored when “spinning up” a constant inductor L from $i(0) = 0$ A to current $i(T) = I$:

$$\begin{aligned}
 E &= \int_{t=0}^T p(t) dt = \int_{t=0}^T i(t) \cdot v(t) dt \\
 &= \int_{t=0}^T i(t) \cdot L \frac{di}{dt} dt = L \int_{i=0}^I i di \\
 &= L \left(\frac{1}{2} i^2 \right) \bigg|_{i=0}^I = L \left(\frac{1}{2} I^2 \right) = \frac{1}{2} L I^2.
 \end{aligned}$$

6/3/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

15



Inductive Reactance

- This will be important later...
- Under an AC excitation with frequency f , an inductor has a reactance of:

$$X_L = 2\pi f L \Omega$$

- The + sign means → an inductor's voltage *leads* its current by a phase angle of $\pi/2$.
 - We'll discuss what this means later...
