




**FAMU-FSU**  
**College of Engineering**



**Lecture #9:**  
**AC Network Analysis**  
**(Part III)**

**EEL 3003**  
**Introduction to Electrical Engineering**  
**Summer Semester, 2013**  
**Instructor: Dr. Michael Frank**

6/11/2013 M. Frank, EEL 3003 - Intro. EE, Summer 2013 1



**FAMU-FSU College of Engineering**

**Administrative Announcements**

- Outline of today's class session:
  1. Finish Chapter 4, AC Network Analysis
    - §4.4 – Phasor Solution of Circuits with Sinusoidal Excitation
    - §4.5 – AC Circuit Analysis Methods
- Homework reminder:
  - Read Ch. 4 & practice w. these exercises:
    - 4.1\*, 4.12\*, 4.31, 4.59\*, 4.66, 4.68, 4.71, 4.77\*
  - Quiz will be this Thursday (June 13<sup>th</sup>).



## §4.4 – Phasor Solution of Circuits with Sinusoidal Excitation

- An abstract method for solving dynamic, linear circuits
  - Made of ideal resistors, capacitors, & inductors
- Given sinusoidal excitation of the circuit by current/voltage sources at a single frequency
  - But, this method extends to other periodic sources using Fourier decomposition & superposition
    - We may or may not have time to get that deep into it...




phasor ≠ Star Trek phaser

6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

3

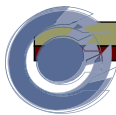

## Review of Complex Numbers

- Why complex numbers?
  - Technical answer (in abstract algebra lingo):
    - The complex number system is *the unique* associative, commutative division algebra that is closed under addition, multiplication, and exponentiation.
      - I.e., it's not just some arbitrary made-up system; it's fundamental!
      - No other set of rules can "complete" the system of real arithmetic

cf. Frobenius theorem

$$j \equiv \sqrt{-1}$$

(imaginary unit)

$$z = a + jb$$

(complex number)

$$\operatorname{Re}[a + jb] = a$$

$$\operatorname{Im}[a + jb] = b$$

(real and imaginary parts)

$$\angle \theta = e^{j\theta} = \cos \theta + j \cdot \sin \theta$$


(Euler's formula)

$$(a + jb)^* = a - jb$$

(definition of complex conjugate)

$$|a + jb| = \sqrt{a^2 + b^2}$$

(definition of norm)

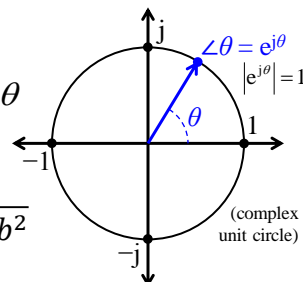

(complex unit circle)

(complex plane)

6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

4



## Conversion Between Rectangular & Polar Form of Complex Numbers

### □ Rectangular form (real & imaginary parts):

■  $z = (a + jb)$

□  $a = \text{Re}[z] = m \cos \theta$  - The real part of  $z$ .

□  $b = \text{Im}[z] = m \sin \theta$  - The imaginary part of  $z$ .

### □ Polar form (phase-magnitude representation):

■  $z = m \cdot e^{j\theta}$

□  $m = |z| = \sqrt{a^2 + b^2}$

■ Magnitude, modulus, norm, amplitude, absolute value of  $z$

□  $\theta = \arg z = \text{atan2}(a, b) = 2 \tan^{-1} \frac{b}{m+a}$       When  $a > 0$ ,  
 $\theta = \tan^{-1}(b/a)$

■ The argument, angle, phase of  $z$ .



## Complex Addition & Multiplication

### □ Given complex numbers:

■  $z_1 = a_1 + jb_1 = m_1 e^{j\theta_1} = m_1 \angle \theta_1$ ,

■  $z_2 = a_2 + jb_2 = m_2 e^{j\theta_2} = m_2 \angle \theta_2$ ,

### □ Addition and multiplication of them works like so:

■ Addition is like vector addition:

□  $z_1 + z_2 = (a_1 + a_2) + j(b_1 + b_2)$

■ To multiply, multiply magnitudes & add angles:

□  $z_1 z_2 = m_1 e^{j\theta_1} m_2 e^{j\theta_2} = (m_1 m_2) e^{j(\theta_1 + \theta_2)} = m_1 m_2 \angle (\theta_1 + \theta_2)$

□ Or in terms of components:

■  $z_1 z_2 = (a_1 + jb_1)(a_2 + jb_2) = (a_1 a_2 - b_1 b_2) + j(a_1 b_2 + b_1 a_2)$




## Complex Division

- Given a complex number
  - $z = a + jb = me^{j\theta} = m\angle\theta,$
- Its reciprocal (multiplicative inverse) is:
  - $z^{-1} = \frac{1}{m}e^{-j\theta} = \frac{z^*}{m^2} = \frac{a-jb}{a^2+b^2}$
- To divide two complex numbers  $z_1/z_2$ ,
  - Divide their magnitudes and subtract their angles:
    - $\frac{z_1}{z_2} = \frac{m_1 e^{j\theta_1}}{m_2 e^{j\theta_2}} = \frac{m_1}{m_2} e^{j(\theta_1 - \theta_2)} = (m_1/m_2)\angle(\theta_1 - \theta_2)$
    - Or in terms of components:
      - $\frac{z_1}{z_2} = \frac{z_1 z_2^*}{m_2^2} = \frac{(a_1 + jb_1)(a_2 - jb_2)}{a_2^2 + b_2^2} = \frac{(a_1 a_2 + b_1 b_2) - j(a_1 b_2 - b_1 a_2)}{a_2^2 + b_2^2}$

6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

7

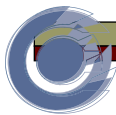

## Phasors

- Suppose you have a general sinusoidal signal (current or voltage):

$$x(t) = A \cos(\omega t + \theta)$$

- Then  $x(t)$  is fully determined by its frequency  $\omega$  and the complex number  $\mathbf{X} = A\angle\theta = Ae^{j\theta}$ .

$$\begin{aligned} x(t) &= A \cos(\omega t + \theta) = \text{Re}[A \cos(\omega t + \theta) + jA \sin(\omega t + \theta)] \\ &= \text{Re}[Ae^{j(\omega t + \theta)}] = \text{Re}[Ae^{j\omega t + j\theta}] = \text{Re}[Ae^{j\omega t} e^{j\theta}] \\ &= \text{Re}[(Ae^{j\theta})e^{j\omega t}] = \text{Re}[\mathbf{X}e^{j\omega t}] \end{aligned}$$

$\mathbf{X}$  is sometimes  
written as  $\mathbf{X}(j\omega)$

6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

8



## Adding Sinusoids Using Phasors


- Given two sinusoidal voltage sources  
 $v_1(t) = V_1 \cos(\omega t + \theta_1)$  and  $v_2(t) = V_2 \cos(\omega t + \theta_2)$  at the same frequency  $\omega$ , find their sum  $v(t) = v_1 + v_2$ .
- Solution: Just add their phasors!  $\mathbf{V}_1 = V_1 \angle \theta_1$ ,  $\mathbf{V}_2 = V_2 \angle \theta_2$   
 ■ This works because:  $\mathbf{V} = V \angle \theta = \mathbf{V}_1 + \mathbf{V}_2$

$$v(t) = v_1(t) + v_2(t)$$

$$= \text{Re}[\mathbf{V}_1 e^{j\omega t} + \mathbf{V}_2 e^{j\omega t}]$$

$$= \text{Re}[(\mathbf{V}_1 + \mathbf{V}_2) e^{j\omega t}]$$

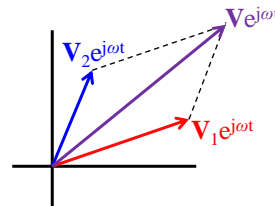
$$= \text{Re}[\mathbf{V} e^{j\omega t}]$$



6/11/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

9

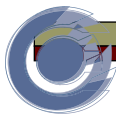
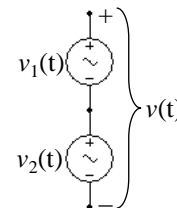
## Adding Sinusoids Example


- Suppose we have the following two AC voltage sources in series:
  - $v_1(t) = (2 \text{ V}) \cos(\omega t + \pi/3)$
  - $v_2(t) = (3 \text{ V}) \cos(\omega t + \pi/2)$
- What is their sum,
  - $v(t) = v_1(t) + v_2(t)$ ,
- expressed as a simple sinusoidal function?
- *Do this as an in-class exercise...*



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013


10

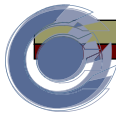
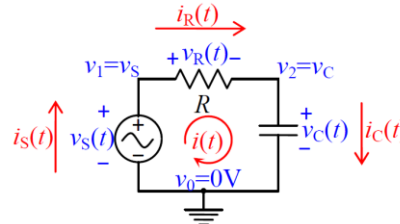
## Practice Exercise #1

□ Do this at home...

- In the previous lecture,
  - see also supplemental “Notes on Solving AC Circuits”
- we solved the differential equations for this circuit and got this equation for  $v_C(t)$ :



$$v_C(t) = \frac{V}{1 + (\omega RC)^2} \sin \omega t - \frac{V\omega RC}{1 + (\omega RC)^2} \cos \omega t$$

- Now, if  $V = 9\text{V}$ ,  $f = 100\text{ Hz}$ ,  $R = 1\text{ k}\Omega$ , and  $C = 1\text{ }\mu\text{F}$ ,
1. Use phasors to express  $v_C(t)$  using a *single* sinusoidal function.
  2. By how many degrees does  $v_C(t)$  lag behind  $v_s(t)$ ?

6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

11



## Superposition of AC Signals

- What if not all of the AC sources in a circuit are at the same frequency?
- We can still solve the circuit, using the superposition principle, as follows:
    - Solve the circuit separately for each source
      - Zeroing out the other sources
    - Add together the solutions

6/11/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

12


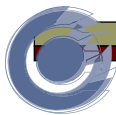
## Impedance

- A complex-valued extension of the concept of resistance, for AC circuits:  $\mathbf{Z} = \mathbf{V}/\mathbf{I}$  (phasors)
  - Captures how capacitors & inductors can impede (in the sense of delay) the phase of AC signals
    - in addition to how resistors directly impede (in the sense of resist) the flow of current
- Impedance  $\mathbf{Z} = R + jX$  breaks down as:
  - Real part  $R = \text{Re}[\mathbf{Z}] = \text{Resistance}$  (always +).
  - Imag. part  $I = \text{Im}[\mathbf{Z}] = \text{Reactance}$  (+ or -).



## Impedance of a Resistor


- WLOG, assume voltage phasor of signal source is:
  - $\mathbf{V}_S = V\angle 0$  (set phase of source = 0)
- For a resistor:
  - $\mathbf{V} = V\angle 0, \mathbf{I} = \frac{V}{R}\angle 0, \therefore$

$$\mathbf{Z} = \frac{V\angle 0}{(V/R)\angle 0} = R\angle 0 = R \text{ (real)}$$


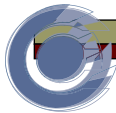
## Impedance of an Inductor

- Recall diff. eq. of inductor:  $v(t) = L \frac{di(t)}{dt}$ .
- For  $\mathbf{V} = V \angle 0$ ,  $v(t) = V \cos \omega t$ .
  - Thus,  $i(t) = \frac{V}{\omega L} \sin \omega t = \frac{V}{\omega L} \cos(\omega t - \pi/2)$ ,
  - so  $\mathbf{I} = \frac{V}{\omega L} \angle -\frac{\pi}{2}$ .
- Thus, an inductor's impedance is:
 
$$\mathbf{Z} = \frac{V \angle 0}{(V/\omega L) \angle -\pi/2} = \omega L \angle \frac{\pi}{2} = j\omega L \text{ (imag.)}$$
  - Thus, the reactance of an inductor is  $X = \omega L$ .



## Impedance of a Capacitor

- Recall diff. eq. of capacitor:  $i(t) = C \frac{dv(t)}{dt}$ .
- For  $\mathbf{V} = V \angle 0$ ,  $v(t) = V \cos \omega t$ .
  - Thus,  $i(t) = -\omega CV \sin \omega t = \omega CV \cos(\omega t + \pi/2)$ ,
  - so  $\mathbf{I} = \omega CV \angle \pi/2$ .
- Thus, a capacitor's impedance is:
 
$$\mathbf{Z} = \frac{V \angle 0}{\omega CV \angle \pi/2} = \frac{1}{\omega C} \angle -\frac{\pi}{2} = -j \frac{1}{\omega C} = \frac{1}{j\omega C}.$$
  - Thus, the reactance of a capacitor is  $X = -1/\omega C$ .





## Admittance

- The reciprocal of impedance,  $\mathbf{Y} = 1/\mathbf{Z}$ .
  - For a capacitor:  $\mathbf{Y} = j\omega C$ .
  - For an inductor:  $\mathbf{Y} = 1/j\omega L$ .
- Like with impedance, we can break down admittance into real & imaginary parts:

$$\mathbf{Y} = G + jB.$$

- $G$  = (AC version of) conductance

- $B$  = susceptance

$$G = \frac{R}{|Z|^2} = \frac{R}{R^2 + X^2}$$

$$B = \frac{-X}{|Z|^2} = \frac{-X}{R^2 + X^2}$$

- If  $X=0$ ,  $G=1/R$ ; if  $R=0$ ,  $B=-1/X$ .

6/11/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

17


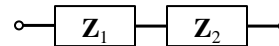
## Combining Elements with Impedance

- For elements in series, their impedances add:




- $\mathbf{Z} = \mathbf{Z}_1 + \mathbf{Z}_2$

- For elements in parallel, their admittances add:

- $\mathbf{Y} = \mathbf{Y}_1 + \mathbf{Y}_2$

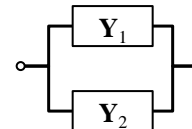
- Thus  $\mathbf{Z} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2}}$



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

18

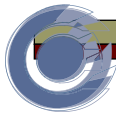


## §4.5 – AC Circuit Analysis Methods

- Here's a general procedure for analyzing all linear circuits excited by AC sources:
  1. Separate sources by frequency (treat separately)
  2. Convert source functions  $v(t)/i(t)$  to phasors  $\mathbf{V}/\mathbf{I}$
  3. Convert all elements to complex impedances.
  4. Solve with usual methods like in ch. 3
    - Simplification of subcircuits via equivalent circuits
    - Node voltage or mesh current analysis  $\rightarrow$  linear eqs.
  5. Convert results from phasor to time-domain form
  6. Superpose solutions for different frequencies

6/11/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

19

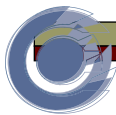

## AC Analysis Example

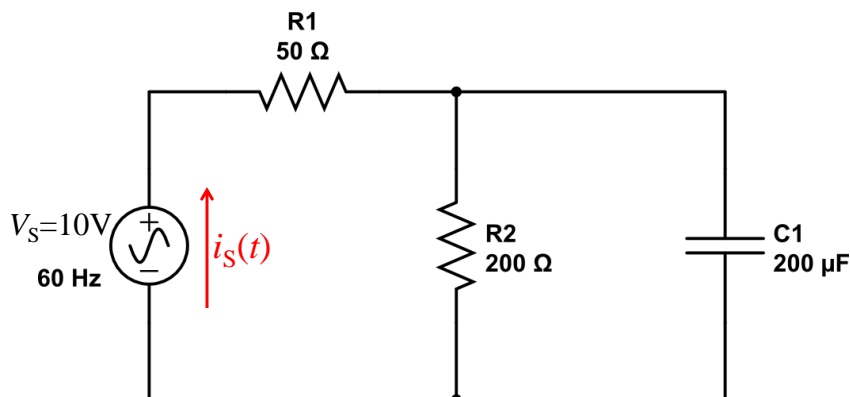- Problem: Find the source current  $i_S(t)$ .



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

20




## 1. Identify source's voltage function & its corresponding phasor

□ Assume source phase is 0 (not otherwise given)

■  $v_S(t) = 10 \cos \omega t$ ;  $\mathbf{V} = 10 \angle 0$ .
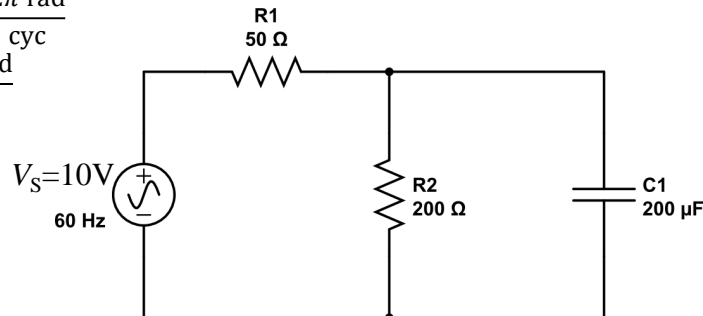
$$\omega = 60 \frac{\text{cyc}}{\text{s}} \cdot \frac{2\pi \text{ rad}}{\text{cyc}} = 377 \frac{\text{rad}}{\text{s}}$$



6/11/2013


M. Frank, EEL 3003 - Intro. EE, Summer 2013

21


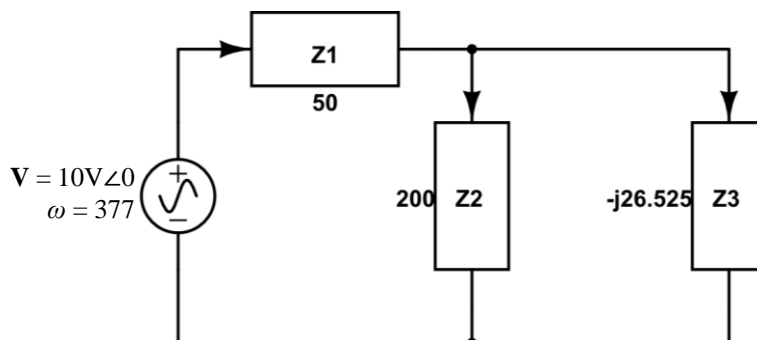
## 2. Express each element as a complex impedance

$$\mathbf{Z}_3 = \frac{1}{j\omega C} = \frac{-j}{(377 \text{ s}^{-1})(100 \mu\text{F})} = -j \cdot 26.526 \Omega$$



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013


22


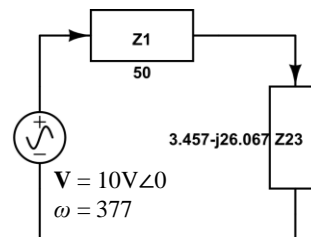
### 3. Simplify circuit by combining elements

- $Z_2$  and  $Z_3$  are in parallel, so we can combine them by adding their admittances:


- $Y_2 = 1/Z_2 = 1/200\Omega = 0.005 \text{ S}$ .
- $Y_3 = 1/Z_3 = j \cdot 0.0377 \text{ S}$
- $Y_2 + Y_3 = (0.005 + j \cdot 0.0377) \text{ S}$
- $Z_2 \parallel Z_3 = 1/(Y_2 + Y_3) = (3.457 - j \cdot 26.067) \Omega$ .



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

23

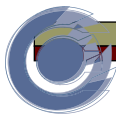

### Circuit simplification continued...

- $Z_1$  and  $Z_{23}$  are in series, so we can combine their impedances by adding them.

- For the overall load:


- $Z = Z_1 + Z_{23}$   
 $= (50 \Omega) + (3.457 - j \cdot 26.067) \Omega$   
 $= (53.457 - j \cdot 26.067) \Omega$

- Now we can apply  $I = V/Z$ :

- $I = (10V \angle 0) / [(53.457 - j \cdot 26.067) \Omega]$   
 $= (0.151 + j \cdot 0.0737) \text{ A} = 0.168 \angle 0.454 \text{ A}$

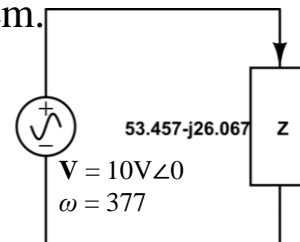0.454 rad  
= 26°

- Thus,  $i_s(t) = (0.168 \text{ A}) \cos(377 t/s + 0.454)$ . □



6/11/2013

M. Frank, EEL 3003 - Intro. EE, Summer 2013

24



## Thévenin/Norton Equivalents of AC Subcircuits

- Again, this is just like the DC case,
  - but with complex impedances in place of resistances.
- Thévenin equivalent circuit:
  - AC voltage source in series with a  $Z$  element.
- Norton equivalent circuit:
  - AC current source in parallel with a  $Z$  element.